

38. (a) Since  $i = \mathcal{E}/(r + R_{\text{ext}})$  and  $i_{\text{max}} = \mathcal{E}/r$ , we have  $R_{\text{ext}} = R(i_{\text{max}}/i - 1)$  where  $r = 1.50 \text{ V}/1.00 \text{ mA} = 1.50 \times 10^3 \Omega$ . Thus,

$$R_{\text{ext}} = (1.5 \times 10^3 \Omega) (1/0.100 - 1) = 1.35 \times 10^4 \Omega.$$

(b)  $R_{\text{ext}} = (1.5 \times 10^3 \Omega) (1/0.500 - 1) = 1.50 \times 10^3 \Omega$ .

(c)  $R_{\text{ext}} = (1.5 \times 10^3 \Omega) (1/0.900 - 1) = 167 \Omega$ .

(d) Since  $r = 20.0 \Omega + R$ ,  $R = 1.50 \times 10^3 \Omega - 20.0 \Omega = 1.48 \times 10^3 \Omega$ .